

Electronics



Nagham Elsayed Mekky

**Faculty of Computer Science and Information
Systems, Mansoura University, Mansoura**


Chapter(3)



Operational Amplifiers

Operational Amplifier

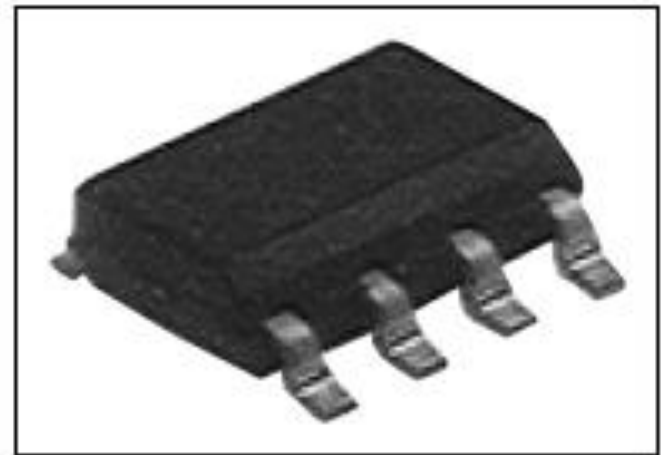- ❑ The op amp is an electronic unit that behaves like a voltage-controlled voltage source.
- ❑ An op amp is an active circuit element designed to perform mathematical operations of addition, subtraction, multiplication, division, differentiation, and integration.
- ❑ Fig.1 shows a typical op amp package.




Figure


A typical operational amplifier.

Operational Amplifier

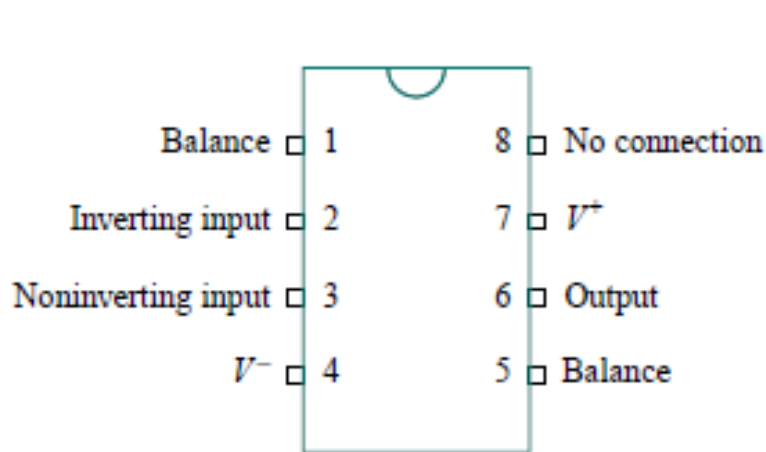- Op amps are commercially available in integrated circuit packages in several forms.
- A typical one is the eight-pin dual in-line package (or DIP), shown in Fig.2(a).



(a)

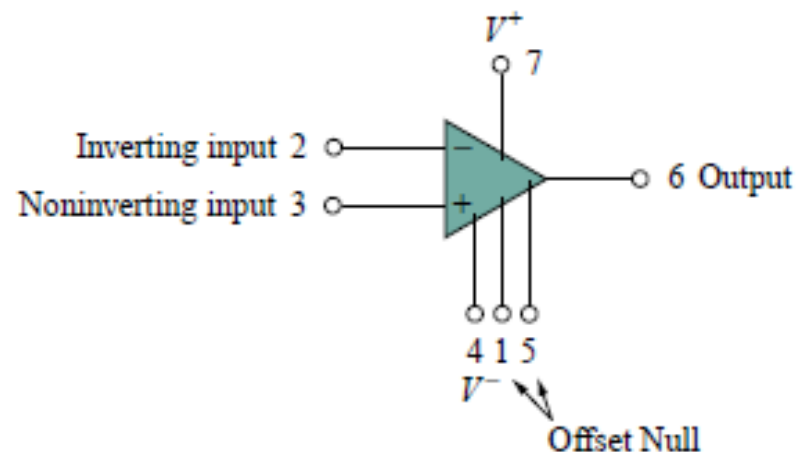

(b)

Figure . A typical op amp: (a) pin configuration, (b) circuit symbol.


Operational Amplifier

- The differential input voltage v_d is given by:

$$v_d = v_2 - v_1$$

- where v_1 is the voltage between the inverting terminal and ground and v_2 is the voltage between the noninverting terminal and ground.

$$v_o = Av_d = A(v_2 - v_1)$$

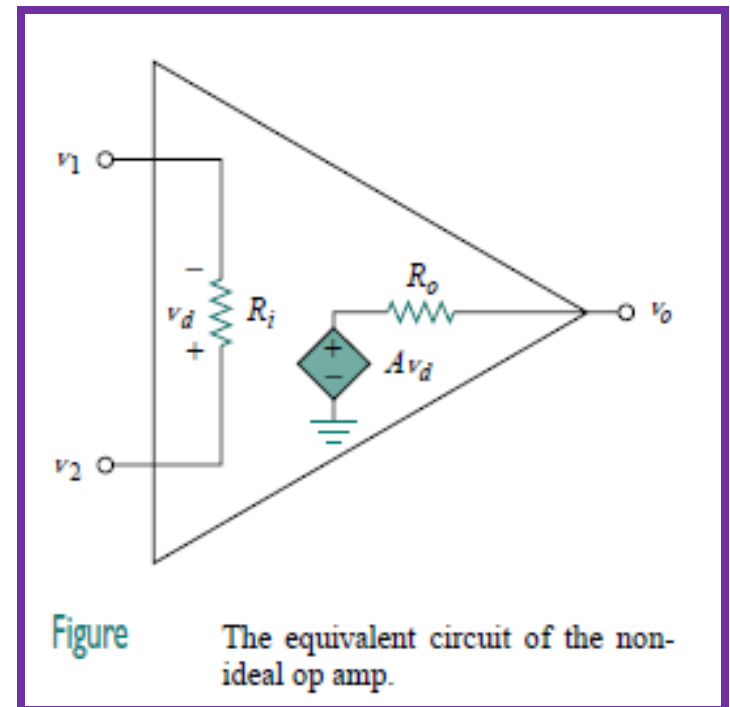

Operational Amplifier

- *A is called the open-loop voltage gain because it is the gain of the op amp without any external feedback from output to input.*

Ideal Op Amp


- An op amp is **ideal** if it has the following characteristics:
 - 1. Infinite open-loop gain, $A = \infty$.
 - 2. Infinite input resistance, $R_i = \infty$.
 - 3. Zero output resistance, $R_o = 0$.
- An **ideal** op amp is an amplifier with infinite open-loop gain, infinite input resistance, and zero output resistance.

Ideal Op Amp

$$i_1 = 0, \quad i_2 = 0$$

$$v_d = v_2 - v_1 \simeq 0$$

$$v_1 = v_2$$

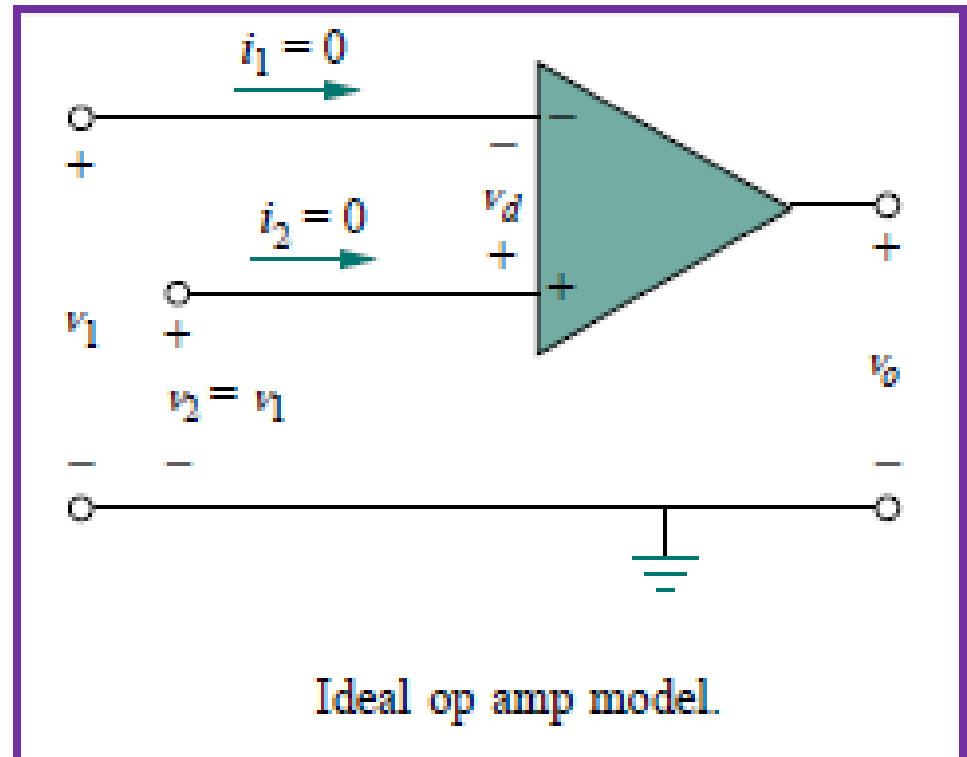

Inverting Amplifier


$$i_1 = i_2 \quad \Rightarrow \quad \frac{v_i - v_1}{R_1} = \frac{v_1 - v_o}{R_f}$$

- But $v_1 = v_2 = 0$ for an ideal op amp, since the noninverting terminal is grounded. Hence,

$$\frac{v_i}{R_1} = -\frac{v_o}{R_f}$$

$$v_o = -\frac{R_f}{R_1} v_i$$

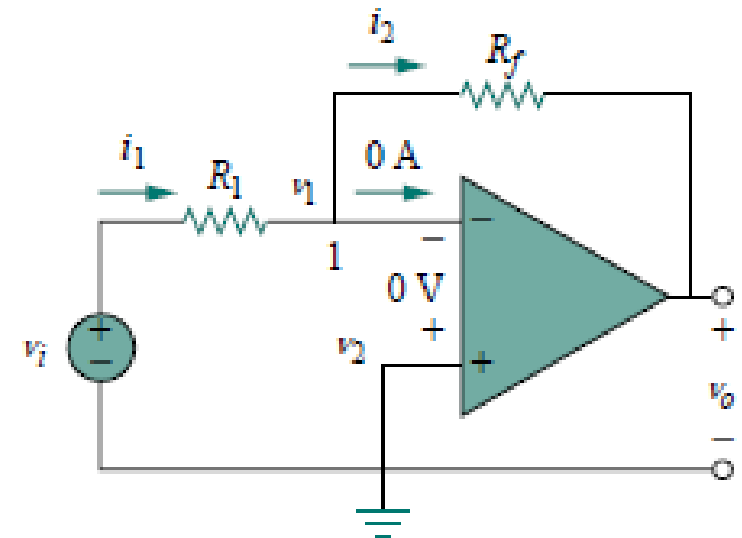- The voltage gain is $A_v = v_o/v_i$
- $= -R_f/R_1$.





Fig

The inverting amplifier.

Inverting Amplifier

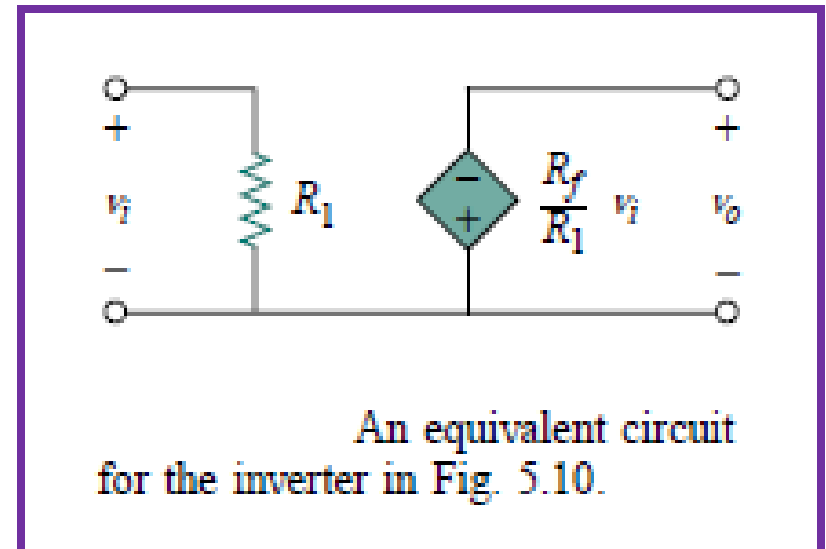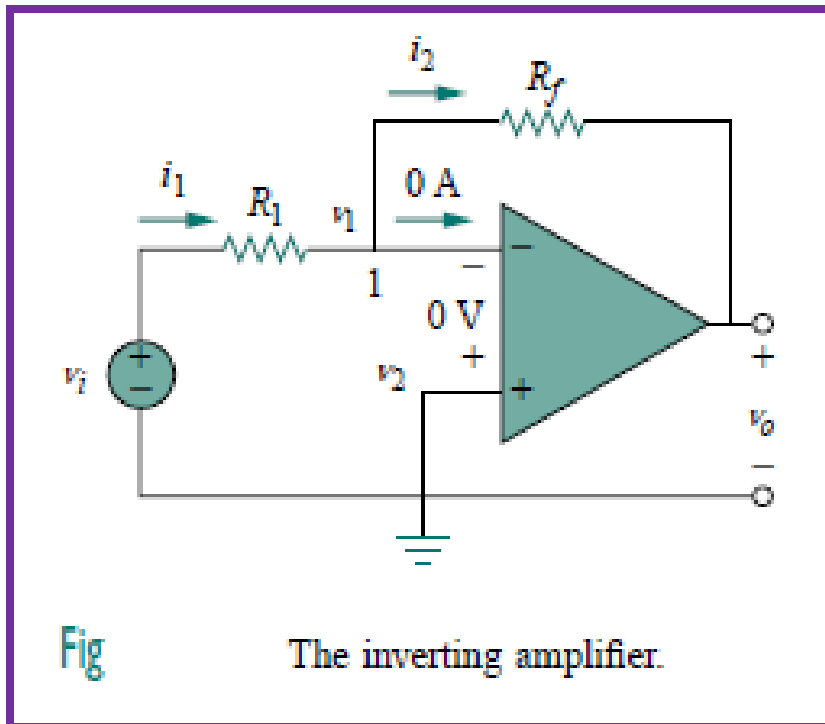
- An **inverting** amplifier reverses the polarity of the input signal while amplifying it.



Noninverting Amplifier

$$i_1 = i_2 \quad \Rightarrow \quad \frac{0 - v_1}{R_1} = \frac{v_1 - v_o}{R_f}$$
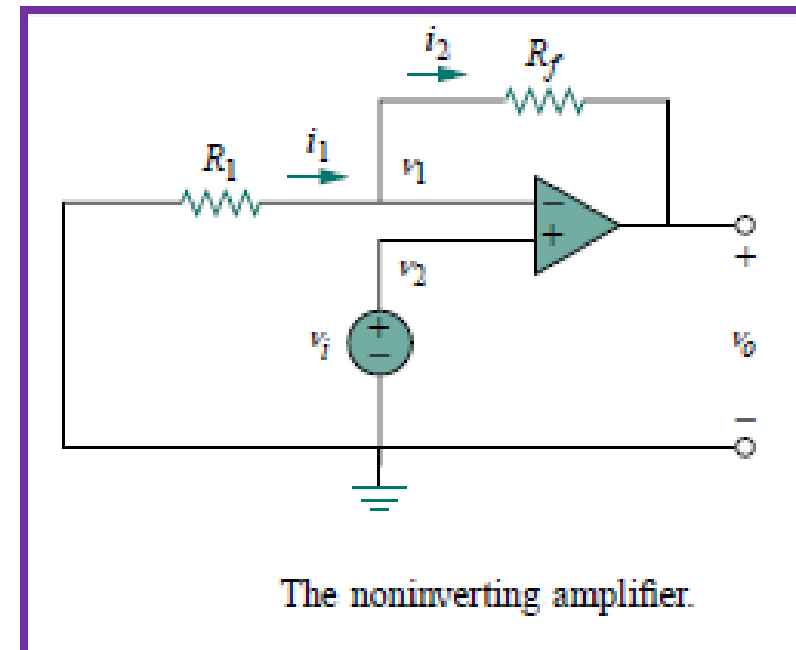
$$v_o = \left(1 + \frac{R_f}{R_1}\right) v_i$$





Noninverting Amplifier

- The voltage gain is $A_v = v_o/v_i = 1 + R_f/R_1$, *which does not have a negative sign*. Thus, the output has the same polarity as the input.
- A **noninverting** amplifier is an op amp circuit designed to provide a positive voltage gain.

Voltage Follower


- Notice that if feedback resistor $R_f = 0$ (short circuit) or $R_1 = \infty$ (open circuit) or both, the gain becomes 1. Under these conditions ($R_f = 0$ and $R_1 = \infty$), the circuit shown is called a *voltage follower* (or *unity gain amplifier*) because the output follows the input. Thus, for a voltage follower

$$v_o = v_i$$

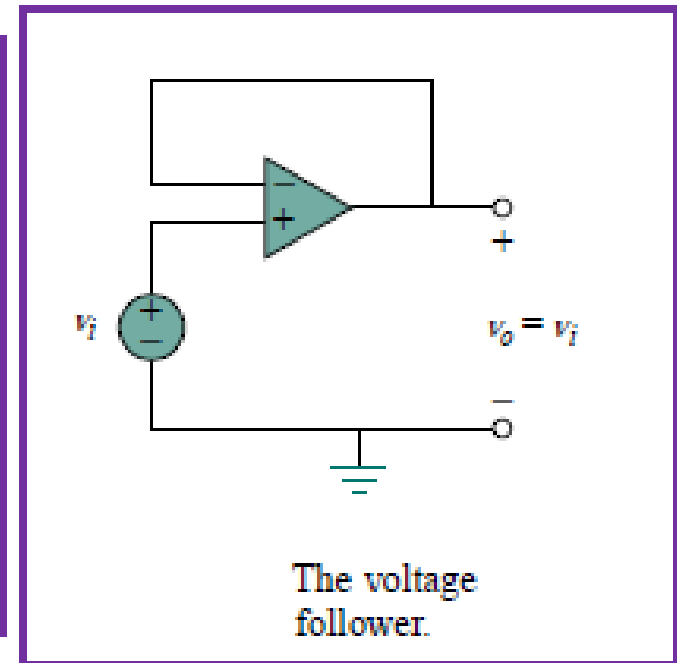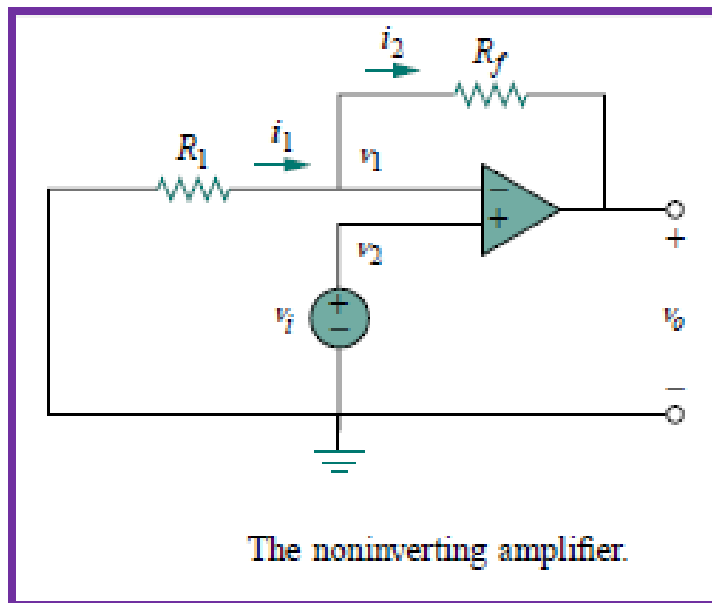


Voltage Follower

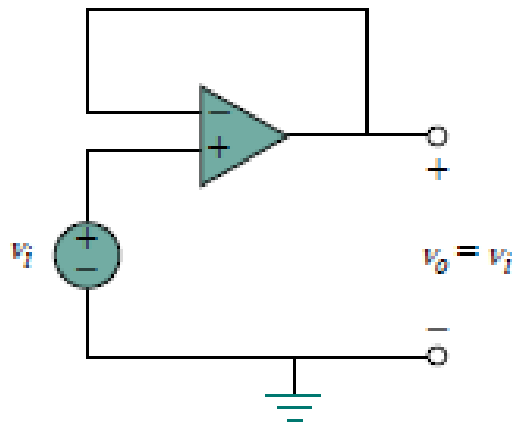- Such a circuit has a very high input impedance and is therefore useful as an intermediate-stage (or buffer) amplifier to **isolate** one circuit from another as shown in Fig. The voltage follower minimizes interaction between the two stages and eliminates interstage loading.



The voltage follower.

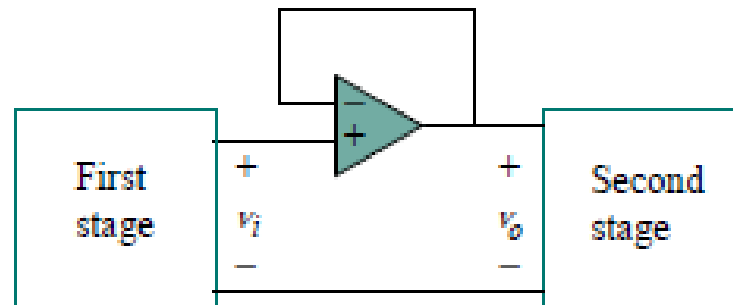

A voltage follower used to isolate two cascaded stages of a circuit.

Summing Amplifier


- A summing amplifier is an op amp circuit that combines several inputs and produces an output that is the weighted sum of the inputs.

$$i = i_1 + i_2 + i_3$$

$$i_1 = \frac{v_1 - v_a}{R_1}, \quad i_2 = \frac{v_2 - v_a}{R_2}$$

$$i_3 = \frac{v_3 - v_a}{R_3}, \quad i = \frac{v_a - v_o}{R_f}$$
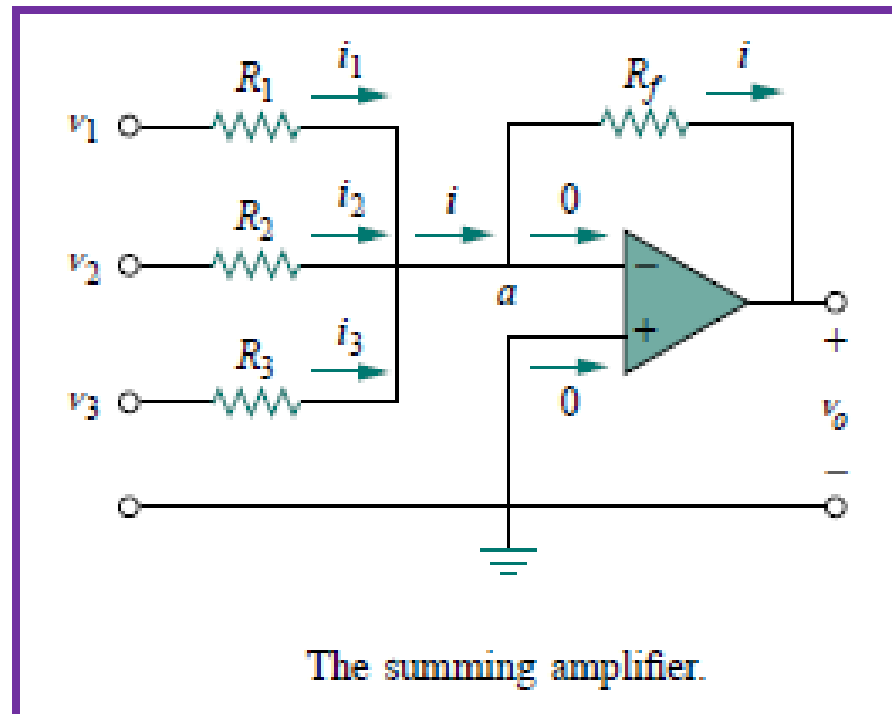
$$v_o = - \left(\frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \frac{R_f}{R_3} v_3 \right)$$




Difference (Differential) Amplifier

- A difference amplifier is a device that amplifies the difference between two inputs.
- Apply KCL at node a:

$$\frac{v_1 - v_a}{R_1} = \frac{v_a - v_o}{R_2}$$
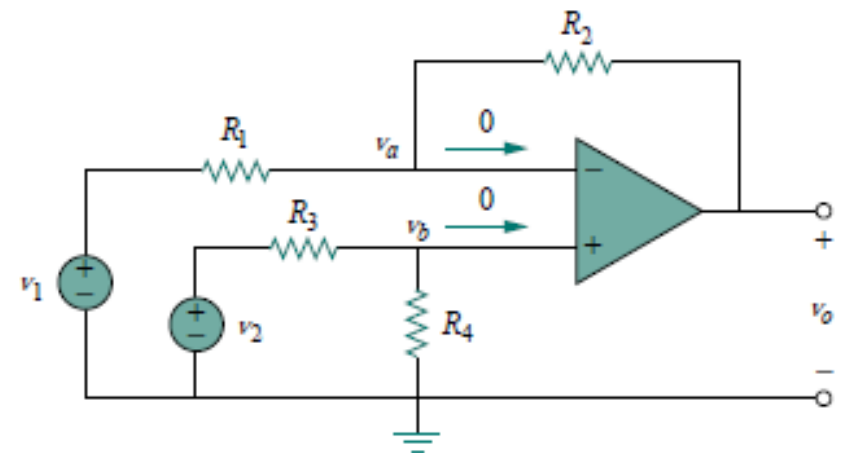
$$v_o = \left(\frac{R_2}{R_1} + 1 \right) v_a - \frac{R_2}{R_1} v_1$$



Difference (Differential) Amplifier


- Apply KCL at node b:

$$\frac{v_2 - v_b}{R_3} = \frac{v_b - 0}{R_4}$$

$$v_b = \frac{R_4}{R_3 + R_4} v_2$$

$$v_a = v_b$$
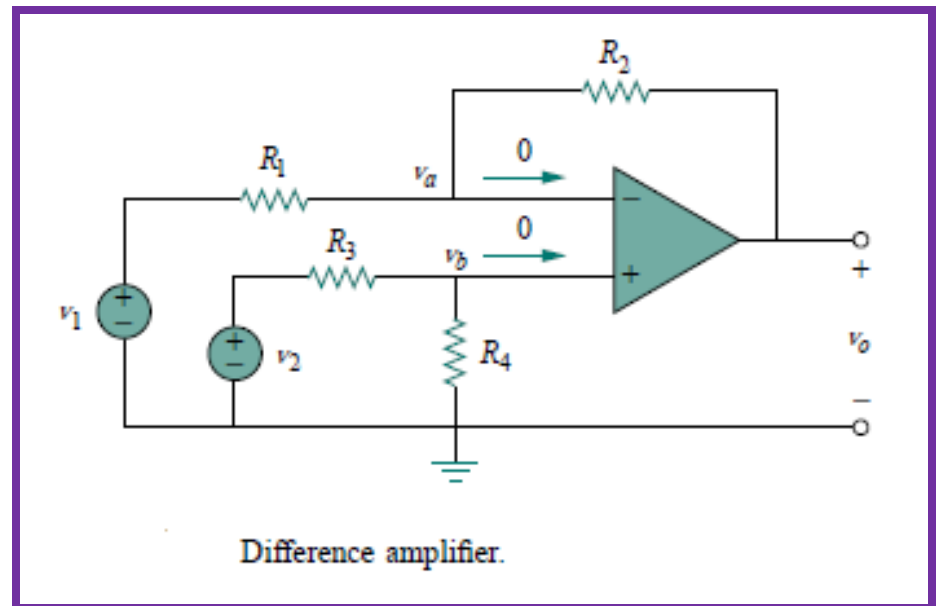
$$v_o = \left(\frac{R_2}{R_1} + 1 \right) \frac{R_4}{R_3 + R_4} v_2 - \frac{R_2}{R_1} v_1$$



Difference (Differential) Amplifier

$$v_o = \frac{R_2 (1 + R_1/R_2)}{R_1 (1 + R_3/R_4)} v_2 - \frac{R_2}{R_1} v_1$$

□ Let

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$

□ When the op amp circuit is a difference amplifier, the equation above becomes,

$$v_o = \frac{R_2}{R_1} (v_2 - v_1)$$

Difference (Differential) Amplifier


- If $R2 = R1$ and $R3 = R4$, the difference amplifier becomes a **subtractor**, with the output:

$$v_o = v_2 - v_1$$

Cascaded Op. Amp. Circuits

- A **cascade** connection is a head-to-tail arrangement of two or more op amp circuits such that the output of one is the input of the next.
- The overall gain of the cascade connection is the product of the gains of the individual op amp circuits,

$$A = A_1 A_2 A_3$$

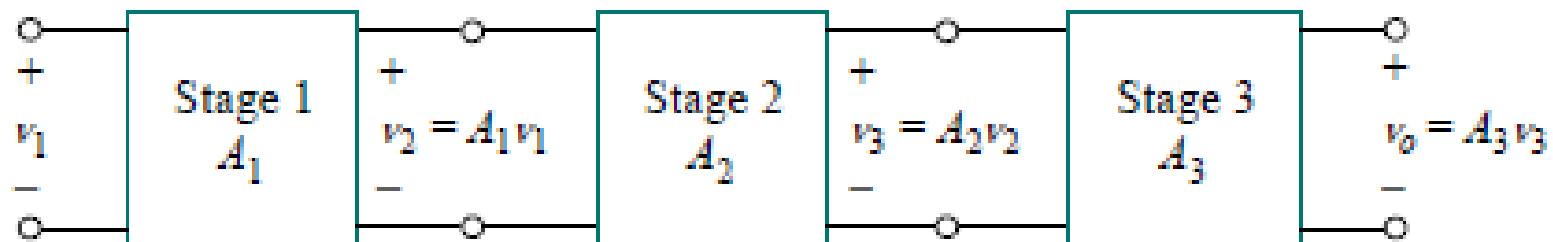


A three-stage cascaded connection.

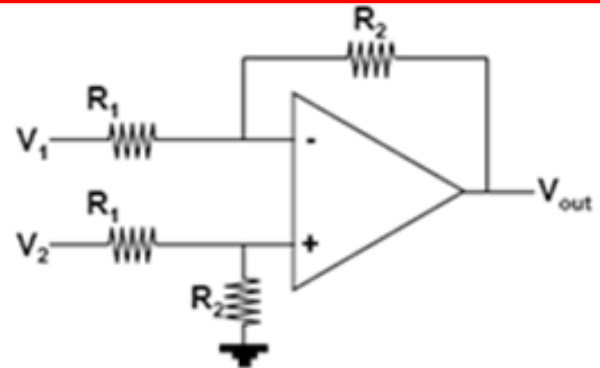
Question:

Differential Amp

$$V_{out} = \frac{R_2}{R_1} (V_2 - V_1)$$




Integrating Amp

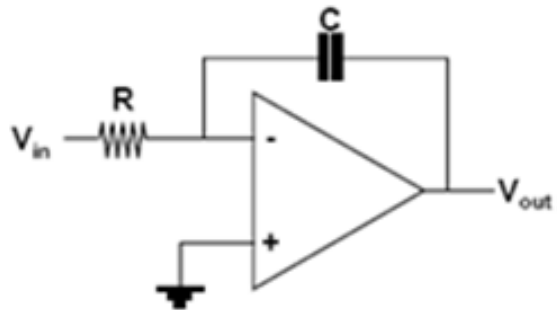

$$V_{out} = -\frac{1}{j\omega CR} V_{in} = -\frac{1}{RC} \int V_{in} dt$$

Differentiating Amp
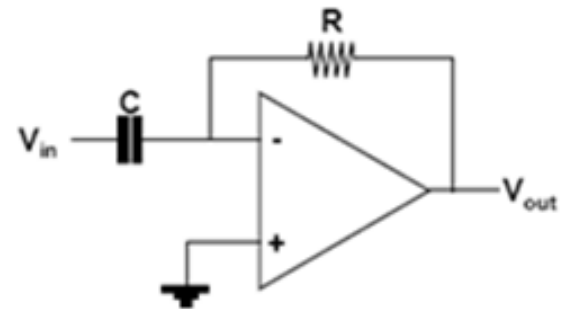
$$V_{out} = -\frac{R}{\frac{1}{j\omega C}} V_{in} = -RC \frac{dV_{in}}{dt}$$





THE END